

 [xfrolk03](#) / [Digital-electronics-1-2021](#)[Code](#)[Issues](#)[Pull requests](#)[Actions](#)[Projects](#)[Wiki](#)[Security](#)[Insights](#)[Settings](#) [main](#) ▾

...

[Digital-electronics-1-2021](#) / [Labs](#) / [04-segment](#) /

xfrolk03 ...

now



..



photo

now



README.md

2 minutes ago

README.md



Lab assignment

1. Preparation tasks (done before the lab at home). Submit:

- Figure or table with connection of 7-segment displays on Nexys A7 board,
- Decoder truth table for common anode 7-segment display.

2. Seven-segment display decoder. Submit:


- Listing of VHDL architecture from source file `hex_7seg.vhd` with syntax highlighting,
- Listing of VHDL stimulus process from testbench file `tb_hex_7seg.vhd` with syntax highlighting and asserts,
- Screenshot with simulated time waveforms; always display all inputs and outputs,
- Listing of VHDL code from source file `top.vhd` with 7-segment module instantiation.

3. LED(7:4) indicators. Submit:

- Truth table and listing of VHDL code for LEDs(7:4) with syntax highlighting,
- Screenshot with simulated time waveforms; always display all inputs and outputs.

1. Preparation tasks

Figure or table with connection of 7-segment displays on Nexys A7 board

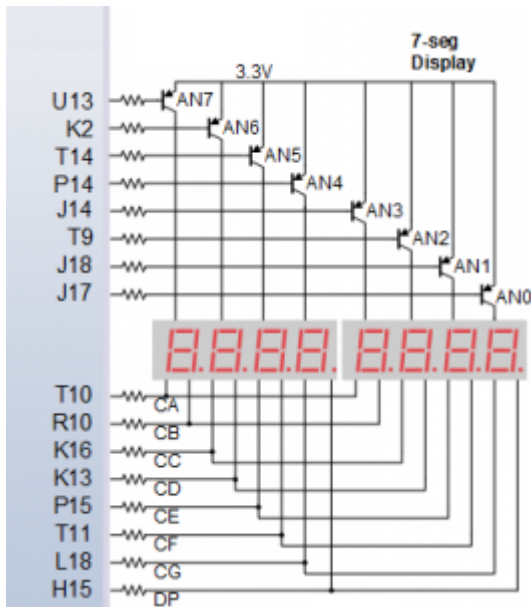

Segment	Connection	Anode	Connection
CA	T10	AN7	U13
CB	R10	AN6	K2
CC	K16	AN5	T14
CD	K13	AN4	P14
CE	P15	AN3	J14
CF	T11	AN2	T9
CG	L18	AN1	J18
DP	H15	AN0	J17

Decoder truth table for common anode 7-segment display

Hex	Inputs	A	B	C	D	E	F	G
0	0000	0	0	0	0	0	0	1
1	0001	1	0	0	1	1	1	1
2	0010	0	0	1	0	0	1	0
3	0011	0	0	0	0	1	1	0

Hex	Inputs	A	B	C	D	E	F	G
4	0100	1	0	0	1	1	0	0
5	0101	0	1	0	0	1	0	0
6	0110	0	1	0	0	0	0	0
7	0111	0	0	0	1	1	1	1
8	1000	0	0	0	0	0	0	0
9	1001	0	0	0	0	1	0	0
A	1010	0	0	0	1	0	0	0
B	1011	1	1	0	0	0	0	0
C	1100	0	1	1	0	0	0	1
D	1101	1	0	0	0	0	1	0
E	1110	0	1	1	0	0	0	0
F	1111	0	1	1	1	0	0	0



2. Seven-segment display decoder

Listing of VHDL architecture from source file `hex_7seg.vhd` with syntax highlighting

```
architecture Behavioral of hex_7seg is
begin
    -----
    -- p_7seg_decoder:
    -- A combinational process for 7-segment display (Common Anode)
    -- decoder. Any time "hex_i" is changed, the process is "executed".
    -- Output pin seg_o(6) controls segment A, seg_o(5) segment B, etc.
```

```

--          a
--      -----
--      f |   | b
--          | g |
--      -----
--      e |   | c
--          |   |
--      -----
--          d
--
-----
p_7seg_decoder : process(hex_i)
begin
    case hex_i is
        when "0000" =>
            seg_o <= "0000001";    -- 0
        when "0001" =>
            seg_o <= "1001111";    -- 1
        when "0010" =>
            seg_o <= "0010010";    -- 2
        when "0011" =>
            seg_o <= "0000110";    -- 3
        when "0100" =>
            seg_o <= "1001100";    -- 4
        when "0101" =>
            seg_o <= "0100100";    -- 5
        when "0110" =>
            seg_o <= "0100000";    -- 6
        when "0111" =>
            seg_o <= "0001111";    -- 7
        when "1000" =>
            seg_o <= "0000000";    -- 8
        when "1001" =>
            seg_o <= "0000100";    -- 9
        when "1010" =>
            seg_o <= "0001000";    -- A
        when "1011" =>
            seg_o <= "1100000";    -- B
        when "1100" =>
            seg_o <= "0110001";    -- C
        when "1101" =>
            seg_o <= "1000010";    -- D
        when "1110" =>
            seg_o <= "0110000";    -- E
        when others =>
            seg_o <= "0111000";    -- F
    end case;
end process p_7seg_decoder;

end Behavioral;

```

**Listing of VHDL stimulus process from testbench file
tb_hex_7seg.vhd with syntax highlighting and asserts**

```


p_stimulus : process
begin
    report "Stimulus process started" severity note;

    s_hex <= "0000"; wait for 100 ns;
    s_hex <= "0001"; wait for 100 ns;
    s_hex <= "0010"; wait for 100 ns;
    s_hex <= "0011"; wait for 100 ns;
    s_hex <= "0100"; wait for 100 ns;
    s_hex <= "0101"; wait for 100 ns;
    s_hex <= "0110"; wait for 100 ns;
    s_hex <= "0111"; wait for 100 ns;
    s_hex <= "1000"; wait for 100 ns;
    s_hex <= "1001"; wait for 100 ns;
    s_hex <= "1010"; wait for 100 ns;
    s_hex <= "1011"; wait for 100 ns;
    s_hex <= "1100"; wait for 100 ns;
    s_hex <= "1101"; wait for 100 ns;
    s_hex <= "1110"; wait for 100 ns;
    s_hex <= "1111"; wait for 100 ns;

    report "Stimulus process finished" severity note;
    wait;
end process p_stimulus;

```

Screenshot with simulated time waveforms

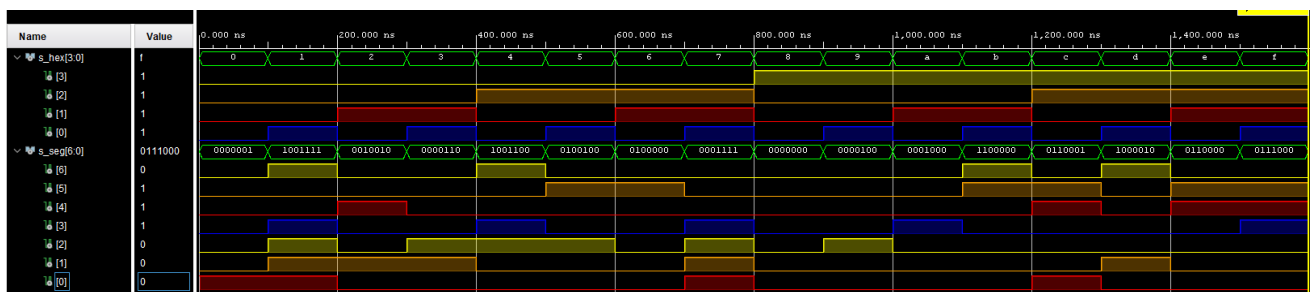

Listing of VHDL code from source file top.vhd with 7-segment module instantiation

```

hex7_seg : entity work.hex_7seg
port map(
    hex_i    => SW,

    seg_o(6) => CA,
    seg_o(5) => CB,
    seg_o(4) => CC,
    seg_o(3) => CD,
    seg_o(2) => CE,
    seg_o(1) => CF,
    seg_o(0) => CG
);

```

LED(7:4) indicators.

Truth table and listing of VHDL code for LEDs(7:4) with syntax highlighting

Hex	Inputs	LED4	LED5	LED6	LED7
0	0000	1	0	0	0
1	0001	0	0	1	1
2	0010	0	0	0	1
3	0011	0	0	1	0
4	0100	0	0	0	1
5	0101	0	0	1	0
6	0110	0	0	0	0
7	0111	0	0	1	0
8	1000	0	0	0	1
9	1001	0	0	1	0
A	1010	0	1	0	0
B	1011	0	1	1	0
C	1100	0	1	0	0
D	1101	0	1	1	0
E	1110	0	1	0	0
F	1111	0	1	1	0

```
-- Turn LED(4) on if input value is equal to 0, ie "0000"
LED(4) <= '1' when SW = "0000" else '0';
-- Turn LED(5) on if input value is greater than 9
LED(5) <= '1' when (SW > "1001") else '0';
-- Turn LED(6) on if input value is odd, ie 1, 3, 5, ...
LED(6) <= '1' when (SW = "0001" or SW = "0011" or SW = "0101" or
                    SW = "0111" or SW = "1001" or SW = "1011" or
                    SW = "1101" or SW = "1111")
                    else '0';
-- Turn LED(7) on if input value is a power of two, ie 1, 2, 4, or 8
LED(7) <= '1' when (SW = "0001" or SW = "0010" or SW = "0100" or
```

```
SW = "1000")
else '0';
```

Screenshot with simulated time waveforms

