

 [xfolrk03](#) / [Digital-electronics-1-2021](#)[Code](#)[Issues](#)[Pull requests](#)[Actions](#)[Projects](#)[Wiki](#)[Security](#)[Insights](#)[Settings](#) [main](#) ▾

...

[Digital-electronics-1-2021](#) / [Labs](#) / [06-display_driver](#) / [README.md](#)

xfolrk03 Update README.md

 1 contributor[Raw](#)[Blame](#)

213 lines (171 sloc) | 6.33 KB

Lab assignment

1. Preparation tasks (done before the lab at home). Submit:

- Timing diagram figure for displaying value 3.142 .

2. Display driver. Submit:


- Listing of VHDL code of the process `p_mux` with syntax highlighting.
- Listing of VHDL testbench file `tb_driver_7seg_4digits` with syntax highlighting and asserts,
- Screenshot with simulated time waveforms; always display all inputs and outputs,
- Listing of VHDL architecture of the top layer.

3. Eight-digit driver. Submit:

- Image of the driver schematic. The image can be drawn on a computer or by hand.

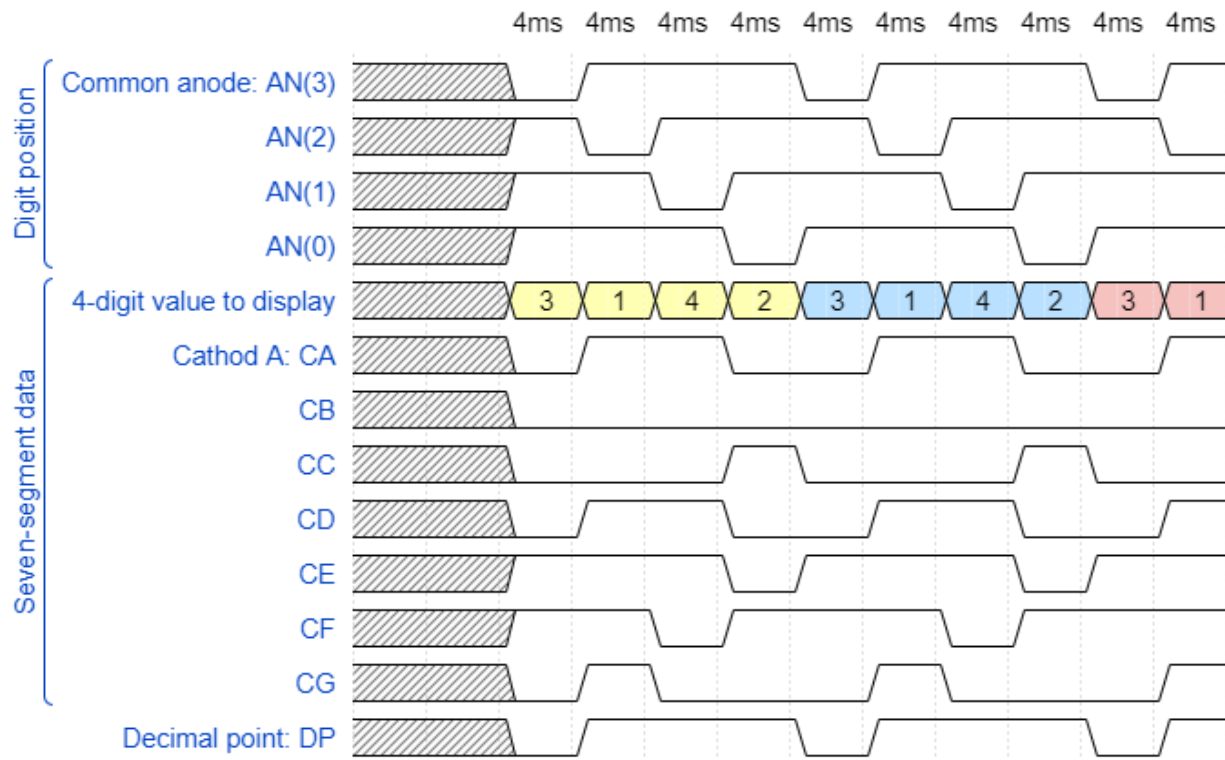1. Preparation tasks

Timing diagram figure for displaying value 3.142



2. Display driver

Listing of VHDL code of the process `p_mux` with syntax highlighting

```
p_mux : process(s_cnt, data0_i, data1_i, data2_i, data3_i, dp_i)
begin
    case s_cnt is
        when "11" =>
            s_hex <= data3_i;
            dp_o <= dp_i(3);
            dig_o <= "0111";

        when "10" =>
            s_hex <= data2_i;
            dp_o <= dp_i(2);
            dig_o <= "1011";

        when "01" =>
            s_hex <= data1_i;
            dp_o <= dp_i(1);
            dig_o <= "1101";

        when others =>
            s_hex <= data0_i;
            dp_o <= dp_i(0);
            dig_o <= "1110";
```

```

        end case;
    end process p_mux;

```

Listing of VHDL testbench file `tb_driver_7seg_4digits` with syntax highlighting and asserts

```

library ieee;
use ieee.std_logic_1164.all;

entity tb_driver_7seg_4digits is
end entity tb_driver_7seg_4digits;

architecture testbench of tb_driver_7seg_4digits is

    constant c_CLK_100MHZ_PERIOD : time      := 10 ns;

    signal s_clk_100MHz : std_logic;

    signal s_reset      : std_logic;

    signal s_data0      : std_logic_vector(4 - 1 downto 0);
    signal s_data1      : std_logic_vector(4 - 1 downto 0);
    signal s_data2      : std_logic_vector(4 - 1 downto 0);
    signal s_data3      : std_logic_vector(4 - 1 downto 0);

    signal s_dp_i       : std_logic_vector(4 - 1 downto 0);
    signal s_dp_o       : std_logic;
    signal s_seg_o       : std_logic_vector(7 - 1 downto 0);

    signal s_dig        : std_logic_vector(4 - 1 downto 0);

begin

    uut_driver_7seg_4digits : entity work.driver_7seg_4digits
        port map(
            clk => s_clk_100MHz,
            reset => s_reset,

            data0_i => s_data0,
            data1_i => s_data1,
            data2_i => s_data2,
            data3_i => s_data3,

            dp_i => s_dp_i,

            dp_o  => s_dp_o,
            seg_o => s_seg_o,
            dig_o => s_dig
        );

    -----
    -- Clock generation process
    -----

```

```

p_clk_gen : process
begin
    while now < 750 ns loop
        s_clk_100MHz <= '0';
        wait for c_CLK_100MHZ_PERIOD / 2;
        s_clk_100MHz <= '1';
        wait for c_CLK_100MHZ_PERIOD / 2;
    end loop;
    wait;
end process p_clk_gen;

-----

-- Reset generation process
-----

p_reset_gen : process
begin
    s_reset <= '0';
    wait for 28 ns;

    s_reset <= '1';
    wait for 53 ns;

    s_reset <= '0';
    wait;
end process p_reset_gen;

-----

-- Data generation process
-----

p_stimulus : process
begin
    report "Stimulus process started" severity note;

    report "Test1" severity note;
    s_data3 <= "0011";
    wait for 10 ns;
    assert (s_seg_o = "0000110")
    report "Test failed" severity error;


    report "Test2" severity note;
    s_data2 <= "0001";
    wait for 10 ns;
    assert (s_seg_o = "1001111")
    report "Test failed" severity error;

    report "Test3" severity note;
    s_data1 <= "0100";
    wait for 10 ns;
    assert (s_seg_o = "1001100")
    report "Test failed" severity error;

    report "Test4" severity note;
    s_data0 <= "0010";
    wait for 10 ns;
    assert (s_seg_o = "0010010")
    report "Test failed" severity error;

```

Screenshot with simulated time waveforms

 

Listing of VHDL architecture of the top layer.

https://github.com/xfrolk03/Digital-electronics-1-2021/blob/main/Labs/06-display_driver/README.md

```

dp_o => DP,

seg_o(6) => CA,
seg_o(5) => CB,
seg_o(4) => CC,
seg_o(3) => CD,
seg_o(2) => CE,
seg_o(1) => CF,
seg_o(0) => CG,

dig_o => AN(4 - 1 downto 0)
);
AN(7 downto 4) <= b"1111";

end architecture Behavioral;

```

3. Eight-digit driver

Image of the driver schematic

